

Name: _____

Chapter 10 Test: Boolean Logic

Q1


Consider this logic expression.

$$X = (A \text{ AND } B) \text{ OR } (B \text{ AND NOT } C)$$

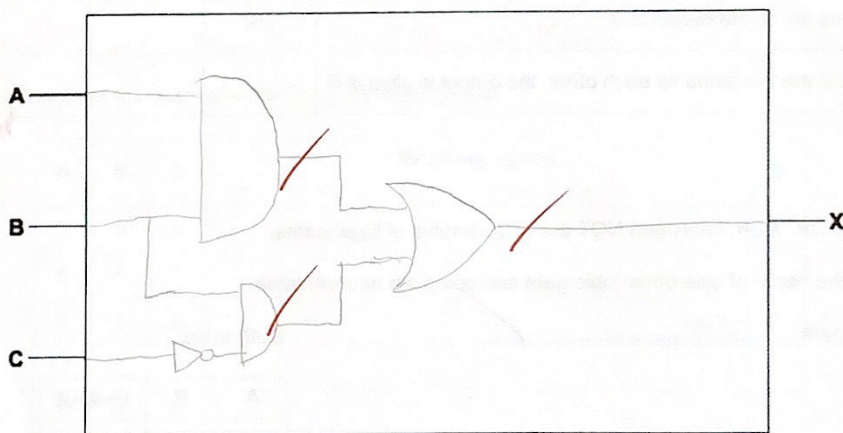- (a) Draw a logic circuit for this logic expression.

Each logic gate must have a maximum of **two** inputs.

Do **not** simplify this logic expression.



4 [4]

- (b) Complete the truth table from the given logic expression.

A	B	C	Working space		X
			$A \wedge B$	$B \wedge C'$	
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	1	0	1

4 [4]

Q2

- 7 NAND, OR and XOR are three types of logic gate.

(a) Four statements are shown about the logic gates.

Tick (✓) to show which statements apply to each logic gate. Some statements may apply to more than one logic gate.

Statement	NAND (✓)	OR (✓)	XOR (✓)
if both inputs are 1, the output is 1		✓	✓
if both inputs are different from each other, the output is 1	✓	✓	✓
if both inputs are 0, the output is 0	✓	✓	✓
if both inputs are the same as each other, the output is always 0			✓

[4]

- (b) NAND, OR, XOR, NOR and NOT are all examples of logic gates.

State the name of **one** other logic gate and complete its truth table.

Logic gate AND


Truth table:

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

[2]

Q3)

Consider the logic circuit:

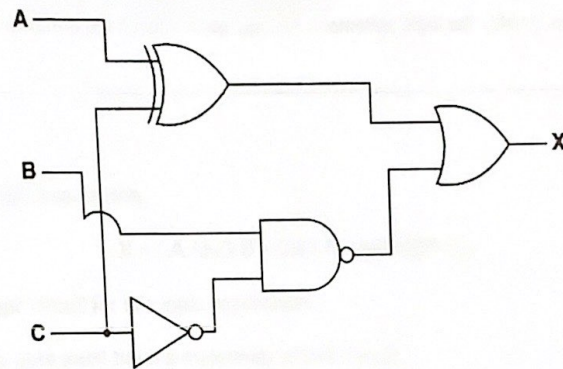

(a) Write a logic statement to match the given logic circuit.

(A XOR C) OR (B NAND (NOT C)) [3]

(b) Complete the truth table for the given logic circuit.

A	B	C	Working space		X
			$A \text{ XOR } C$	$B \text{ NAND } \text{NOT } C$	
0	0	0	0	1	1
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	1	1	1
1	0	0	1	1	1
1	0	1	0	1	1
1	1	0	1	0	1
1	1	1	0	1	1

[4]


Q4)

8 Consider the following logic statement:

$$X = ((A \text{ AND NOT } B) \text{ OR } (\text{NOT } (B \text{ NOR } C))) \text{ AND } C$$

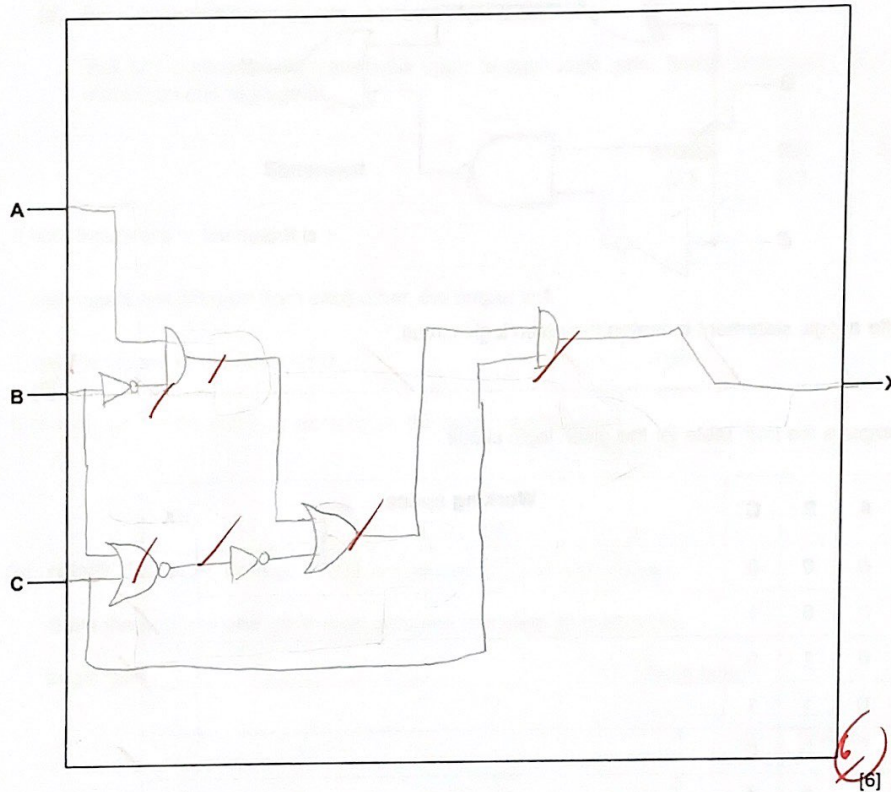(a) Draw a logic circuit to represent the given logic statement.

Do not attempt to simplify the logic statement. All logic gates must have a maximum of two inputs.



[6]

(b) Complete the truth table for the given logic statement.

A	B	C	Working space			X
			$A \text{ AND } B'$	$\text{NOT}(B \text{ NOR } C)$	OR	
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	0	1	1	0
0	1	1	0	1	1	1
1	0	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	0	1	1	0
1	1	1	0	1	1	1

[4]